
Training A

Oscilloscope, Coaxial Cable

Peng, Xingyu 彭星宇

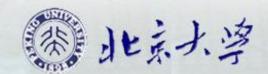


Outline

1. What we learned


- 1.1 basic usage for oscilloscope;
- 1.2 basic property of coaxial cable.


2. What we did

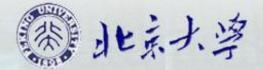- 2.1 Measure the reflection;
- 2.2 Measure the cable length by Oscilloscope;
- 2.3 Delay the signal;
- 2.4 Divide single signal to two signals.




1.1 The basic usage of the Oscilloscope.

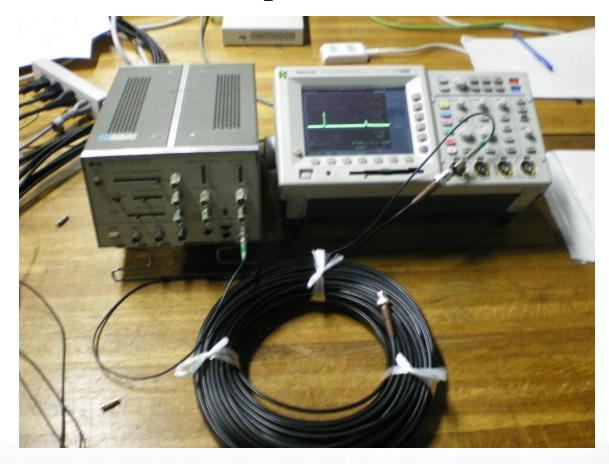

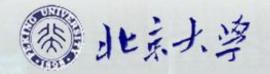


1.2 The basic property of coaxial cable.

Impedance

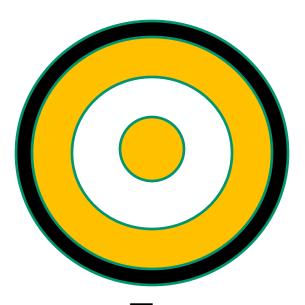


$$Z = \sqrt{\frac{1}{\xi_r}} 60 \ln \frac{b}{a}$$

Impedance matching

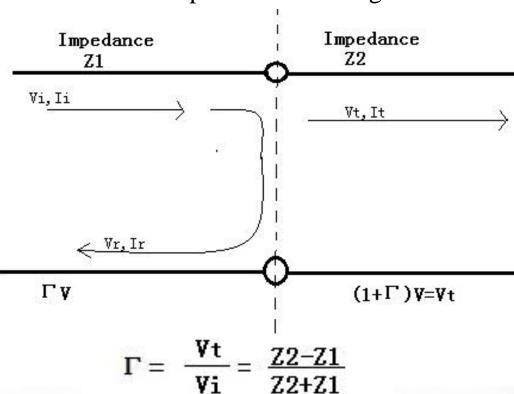

a: diameter of inner conductor


b: inner diameter of outer conductor

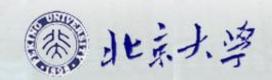



$\mathbb{Z}2=\infty,\Gamma=1$

2.1 Measure the reflection

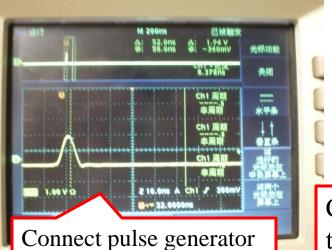

$$\Gamma = \frac{\mathbf{Vt}}{\mathbf{Vi}} = \frac{\mathbf{Z2} - \mathbf{Z1}}{\mathbf{Z2} + \mathbf{Z1}}$$

to oscilloscope with "T"

connector





Connect a long cable to "T" connector and open the end of the long cable

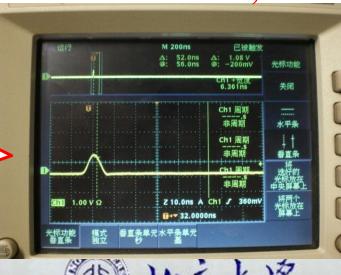Connect the end of the long cable with a 50 Ω termination









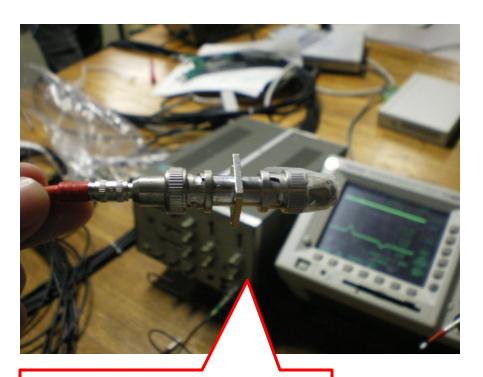

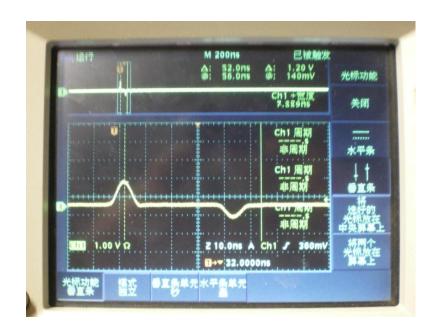
The inner conductor and outer conductor are connected directly.



$$Z2=0,\Gamma=-1$$

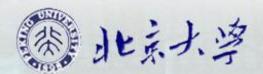

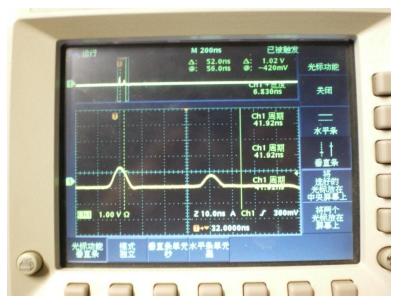2.2 Measure the cable length by Oscilloscope



A 5m cable, Δt1=50ns

The velocity of signal in cable:


$$v = \frac{5m \times 2}{50ns} = 20cm/ns$$



A long cable, $\Delta t = 500$ ns

$$\frac{5m}{L} = \frac{50ns}{500ns}$$


$$L=50m$$

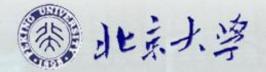





2.3 Delay the signal.



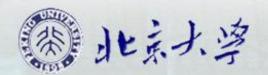

2.4 Divide single signal to two signals.

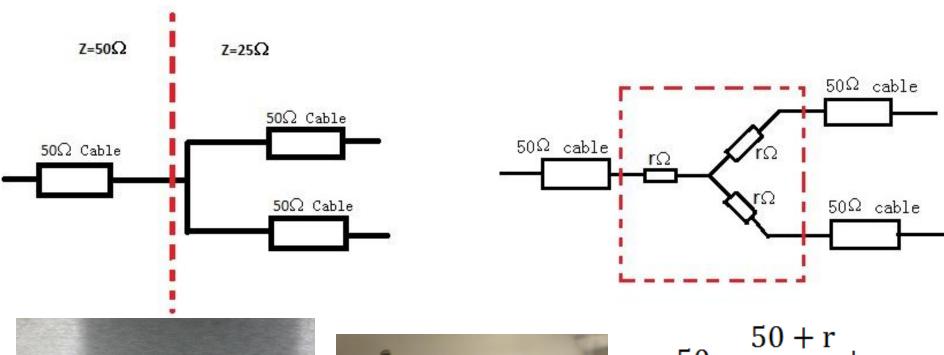


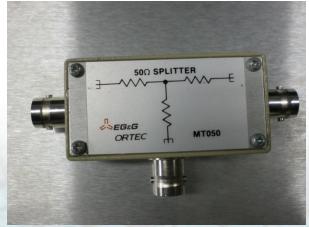






$$50 = \frac{50 + r}{2} + r_{4}$$

$$r = 16.7 \Omega_{4}$$

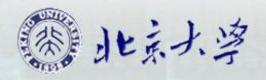

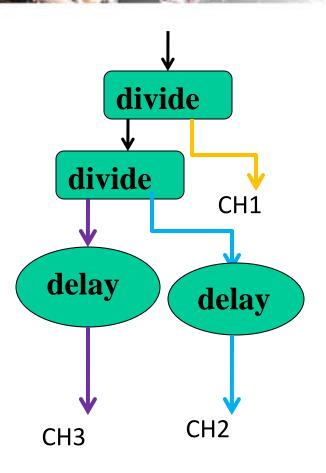

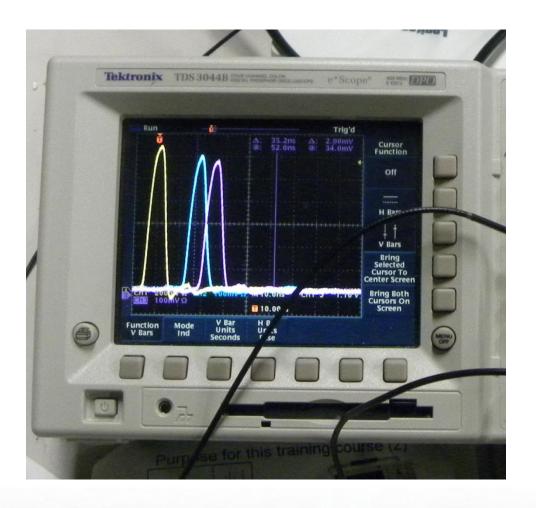

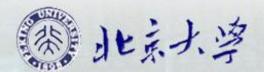

Thanks for your listening!

